



**MAULANA ABUL KALAM AZAD UNIVERSITY OF
TECHNOLOGY, WEST BENGAL**

Paper Code : BCA-101

DIGITAL ELECTRONICS

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own
words as far as practicable.*

GROUP – A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for the following :

10 × 1 = 10

i) The Boolean equation of AND operation is

- | | |
|------------------|-------------------|
| a) $Y = \bar{A}$ | b) $Y = AB$ |
| c) $Y = A + B$ | d) None of these. |

ii) The logical expression $Y = A + AB$ is equivalent to

- | | |
|------------------------|------------------|
| a) $Y = A$ | b) $Y = AB$ |
| c) $Y = \overline{AB}$ | d) $Y = A + B$. |

iii) The BCD equivalent of 57 is

- | | |
|-----------|--------------|
| a) 111001 | b) 01010111 |
| c) 101111 | d) 10001010. |

- x) The race around condition will be avoided by
- a) J-K flip-flop
 - b) S-R flip-flop
 - c) Master-Slave flip-flop
 - d) None of these.

GROUP - B

(Short Answer Type Questions)

Answer any *three* of the following. $3 \times 5 = 15$

- 2. Draw a full adder circuit as combination of 2 half adders.
- 3. State De Morgan's law and prove it for 2 variables.
- 4. a) Evaluate $(7352)_{10} - (9456)_{10}$ using 9's complement.
b) State Duality principle.
- 5. Minimize the following Boolean expression using K-map.
$$F(A, B, C, D) = \sum(0, 1, 3, 6, 8, 10, 11, 13, 15).$$
- 6. Design a 4-bit parallel-in parallel-out (PIPO) shift register.

GROUP - C

(Long Answer Type Questions)

Answer any *three* of the following. $3 \times 15 = 45$

- 7. a) Represent the decimal number 45 in
 - (i) Hexadecimal code
 - (ii) Gray code
 - (iii) BCD code.
- b) Which gates are called universal gates and why ?
- c) Design a 2×4 decoder. Give truth table and draw circuit diagram using basic gates.

- d) Implement the expression using a Multiplexer.

$$F(A, B, C, D) = \sum(0, 1, 4, 5, 7, 9, 11, 13, 15).$$

$$3 + 5 + 4 + 3$$

8. a) What is combinational circuit ?
b) Differentiate between combinational and sequential circuits.
c) Explain the functionality of clocked JK flip-flop. Give truth table and diagram.
d) Convert SR to JK flip-flop. $2 + 3 + 5 + 5$
9. a) What is register ?
b) Design an decimal to binary encoder.
c) What do you mean by Johnson counter ?
10. What do you mean by race around condition in flip-flop ? Design a J-K flip-flop and discuss its operation. Design and explain the functioning of BCD adder circuit. $5 + 5 + 5$
11. Write short notes on any *three* of the following : 3×5
a) Universal Gate
b) Multiplexer
c) PAL and PLA
d) Excitation Table
e) Full adder using Half-adder.
-